

The 220 ohm resistors come from the game pieces (so actually 10K or 680K ohm). If no piece is placed on a square it will not be there. The resistance will vary depending on the piece placed.

